

2LECE1039

SAHIL YADAV

VLSI Circuit Design EC401 Assignment-1

Q:1 for the Configuration shown in fig 1, determine Small-signal resistance R_x and R_y assume $d \neq 0$


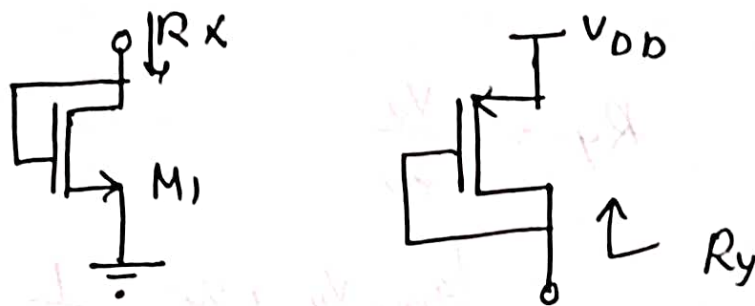



fig 1

Small signal model for (R_x) NMOS

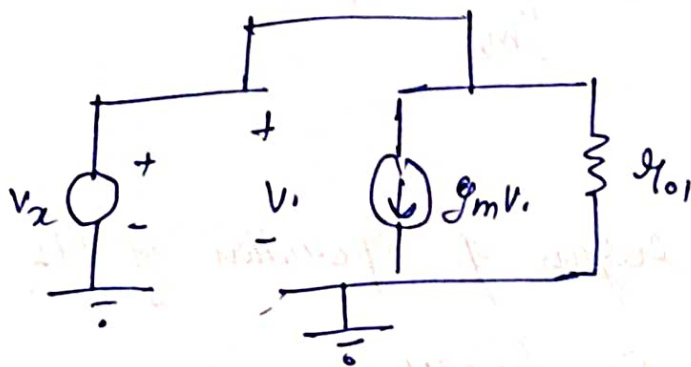

$$\begin{aligned} R_x &= \frac{v_x}{i_x} \\ &= \left(g_m v_x + \frac{v_x}{r_{o1}} \right) \frac{1}{i_x} \\ &= \frac{1}{g_m} \parallel r_{o1} \end{aligned}$$

Small signal model for PMOS CR

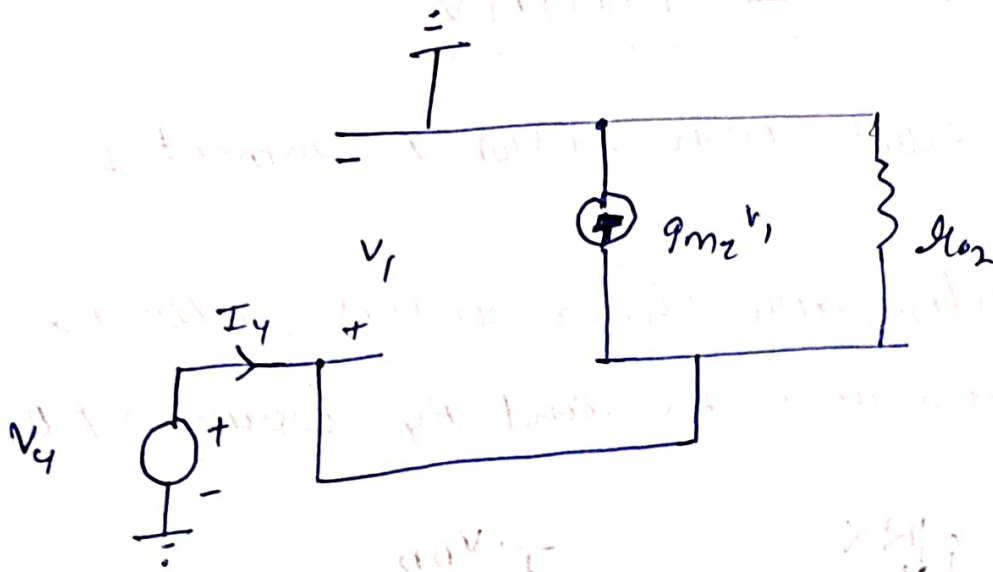


$$R_Y = \frac{V_Y}{I_Y}$$


$$= \left(g_{m2} V_Y + \frac{V_Y}{R_{D2}} \right) \frac{1}{I_Y}$$

$$= \frac{1}{g_{m2}} \parallel R_{D2}$$

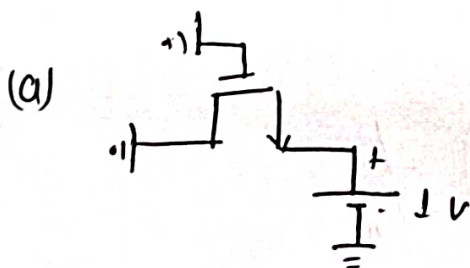
Q: 2 Determine the region of operation of NM in each of circuit shown in figure.



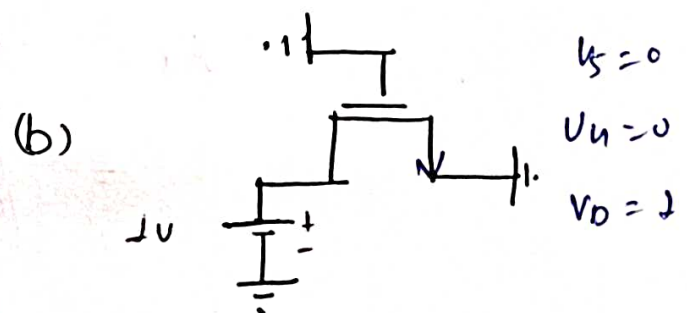$V_{GS} = 0$
 $V_{GS} < V_{TH} \Rightarrow \text{OFF}$



$V_{GS} = 0 \Rightarrow \text{OFF}$

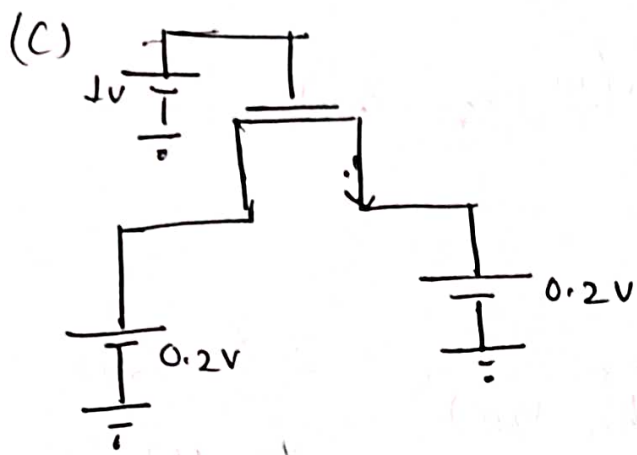


Linear

$$V_{GS} = 0.8 \quad V_{DS} = 0$$

$$V_{GS} > V_{TH}$$

$$V_{DS} < V_{GS} - V_{TH}$$

(d)

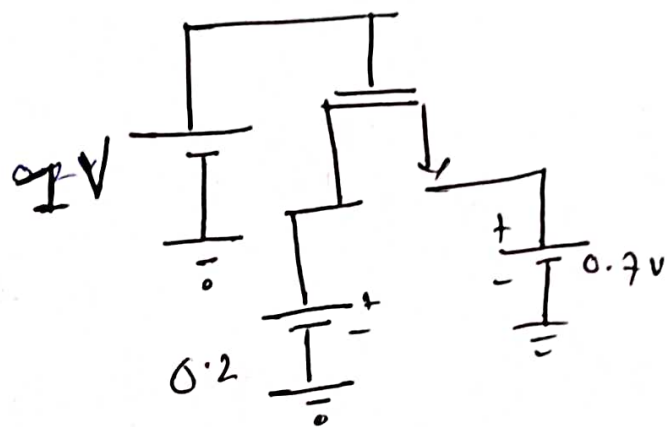

$$V_{th} = 1V$$

$$V_S = 0.7 \quad V_B = 0.2V$$

$$V_{GS} = 0.3 \quad V_{DS} = -0.5V$$

$$V_{th} = 0.6V$$


$$V_{DS} < V_{GS} - V_{th}$$

Linear

$$d=0 \quad V_{th} = 0.4V$$

$$\mu_{n,ox} = 100 \frac{\mu A}{V}$$

Q:3

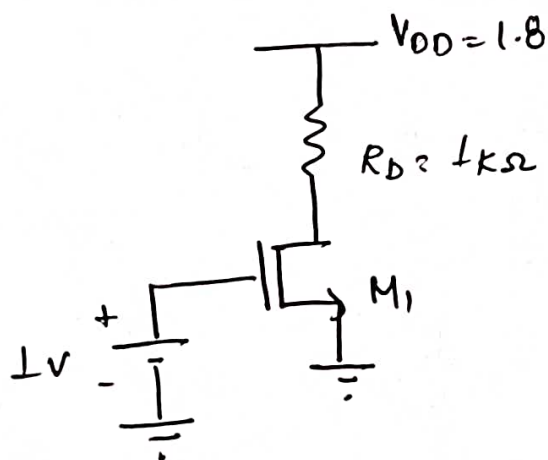

Ans M_1 is at edge of saturation when

$$V_{DS} = V_{GS} - V_{th}$$

$$V_{DS} = (1 - 0.4)V = 0.6V$$

By KCL $I_{D1} = I_{RD} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{1.2V}{1k\Omega} = 1.2mA$

$$\therefore I_D = 1.2 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2$$

$$\Rightarrow \frac{W}{L} = \frac{2 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \frac{2 (1.2 \text{ mA})}{200 \frac{\mu\text{A}}{\text{V}^2} (1 - 0.4)^2}$$

$$\left(\frac{W}{L} \right) \approx 66$$

Q: 4 Calculate the bias current M_1 in Fig 4

if $I = 0.7 \text{ f}$ $R_D = 1 \text{ k}\Omega$ Assuming $\frac{W}{L} = \frac{10}{0.18}$

$\mu_n = 0.1 \text{ V}^{-1}$ and $V_{DD} = 1.8 \text{ V}$, Calculate the Drain Current of M_1 in Fig 4

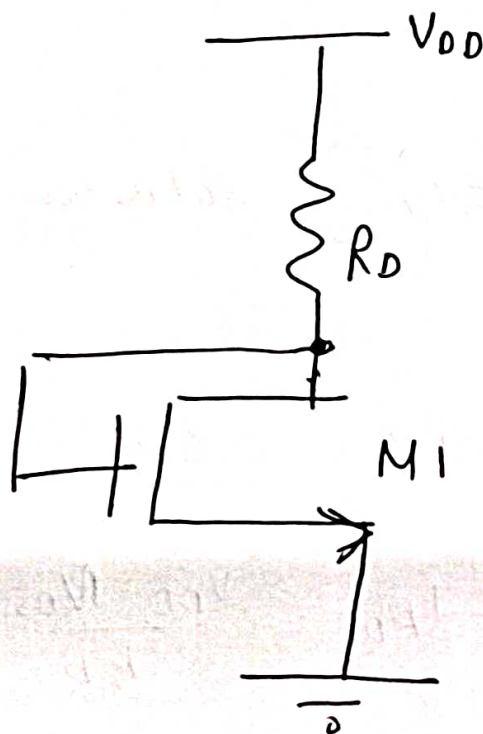
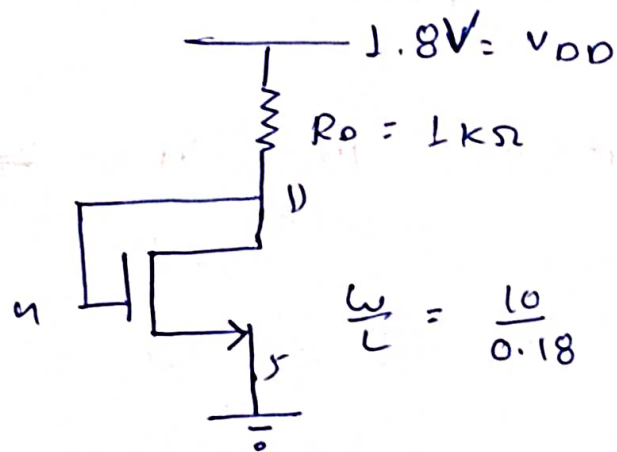


fig 4

Ans (3)Case I $\lambda = 0$ Assumption mos is in Saturation $[V_{GS} - V_{th} < V_{DS}]$ \therefore Since $V_{GS} = V_{DS}$ so always

$$V_{DS} > V_{GS} - V_{th} \Rightarrow V_{DS} > V_{DS} - V_{th}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{th})^2] (1 + \lambda V_{DS})$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [(V_{GS} - V_{th})^2]$$

$$V_{GS} = V_{DS}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [(V_{DS} - V_{th})^2] \quad \text{--- (1)}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{DS} = 1.8 - I_D (1 \times 10^3) \quad \text{--- (2)}$$

Putting values of parameter in Eqⁿ ①

$$I_D = \frac{1}{2} 100 \times 10^{-6} \frac{10}{0.18} (V_{DS} - \cancel{I_D R_D} V_{th})^2$$

After putting Eqⁿ ② in Eq ①

we get

$$\left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 \right) I_D^2 = \left(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{th}) + 1 \right) I_D$$

$$+ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{th})^2 = 0$$

After solving this Quadratic Eqⁿ we get

$$I_D = \left(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{th}) + 1 \right) \pm \sqrt{\left(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{th}) + 1 \right)^2 - 4 \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 (V_{DD} - V_{th})^2 \right)}$$

$$\Rightarrow \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{th}) + 1 \pm \sqrt{\left(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{th}) + 1 \right)^2 - \mu_n C_{ox} \frac{W}{L} R_D^2 (V_{DD} - V_{th})^2}$$

Case II $\lambda = 0.1 \text{ V}^{-1}$

Since M_1 is Diode-Connected it operates in saturation

By KCL $\rightarrow \frac{V_{DD} - V_{th}}{R_D} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{th} - V_{th})^2 (1 + \lambda V_{th})$



By solving above eqⁿ we get

$$V_{th} = 0.807 \text{ V}$$

$$I_D = \frac{V_{DD} - V_{th}}{R_D} \approx 1 \text{ mA}$$

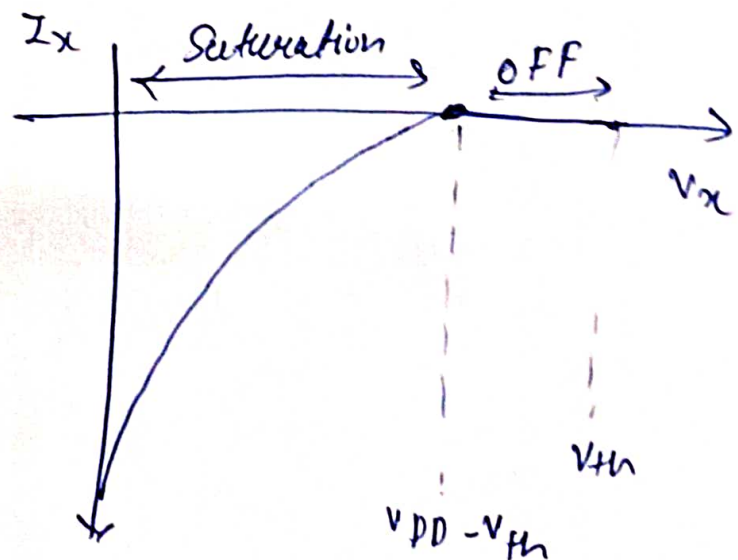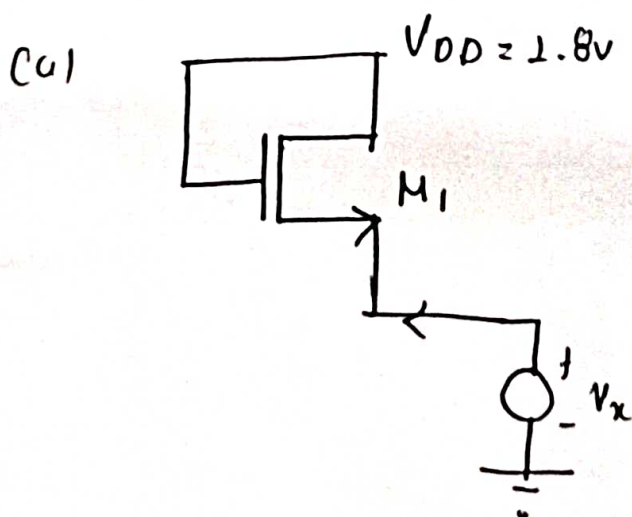Q:5 sketch I_x as a function of v_x for the circuitⁿ shown in fig 5 Assume v_x goes from 0 to $V_{DD} = 1.8$

Also $\lambda = 0$, determine at what value of v_x the device changes its region ~~from~~ of operation.



(b)

