

# 4 BIT Vedic Multiplier

**VLSI Lab-EC403**

Under the supervision of

**Dr .Vasantha MH**

**Presented by**

**SAHIL YADAV [20ECE1039]**

**RAUSHAN KUMAR [20ECE1042]**

**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

17<sup>nd</sup> November 2024

# AIM

- The main aim of this project is to design and simulation of Low power, High Performance Full adder and half adder circuit and measure different parameters 4-bit multiplier and Low-Power, High Performance a) 4 bit Vedic Multiplier and 4 bit multiplier using Cadence tool
- Considering their advantages and disadvantage these are compares on the basis of area, speed and delay


# What is an Multiplier ?

- Multiplication is a mathematical operation that at its simplest is an abbreviated process of adding an integer a specified of times.
- Carries out arithmetic and logic operations on the Operands in computer .

# What is Propagation Delay ?

- The average of time taken for output to change from low level to high level and high level to low level.
- $$T_p = (T_{pHL} + T_{pLH}) / 2$$

# Our Approach ..?

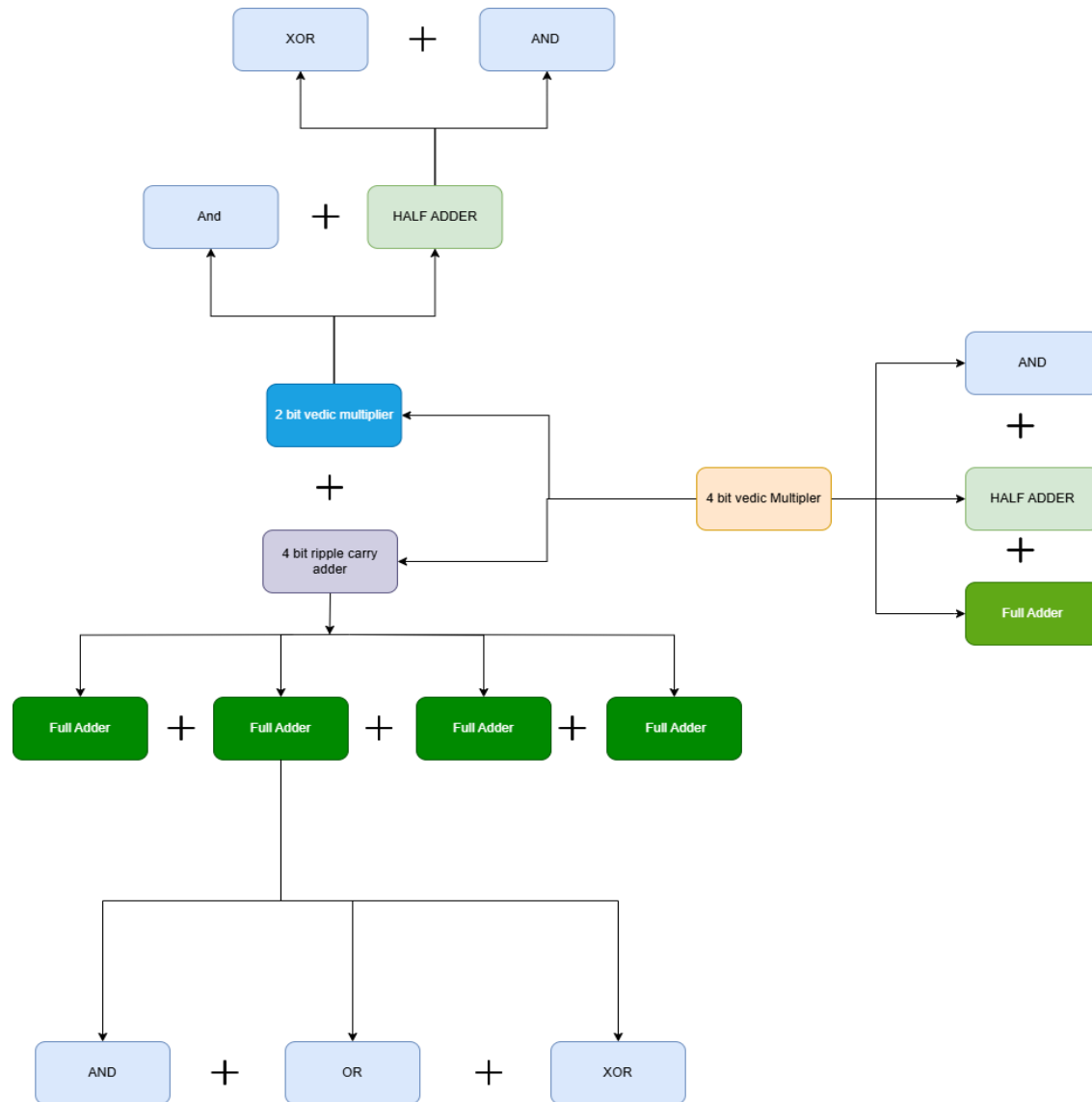

# Inverter:

$$Y=A'$$

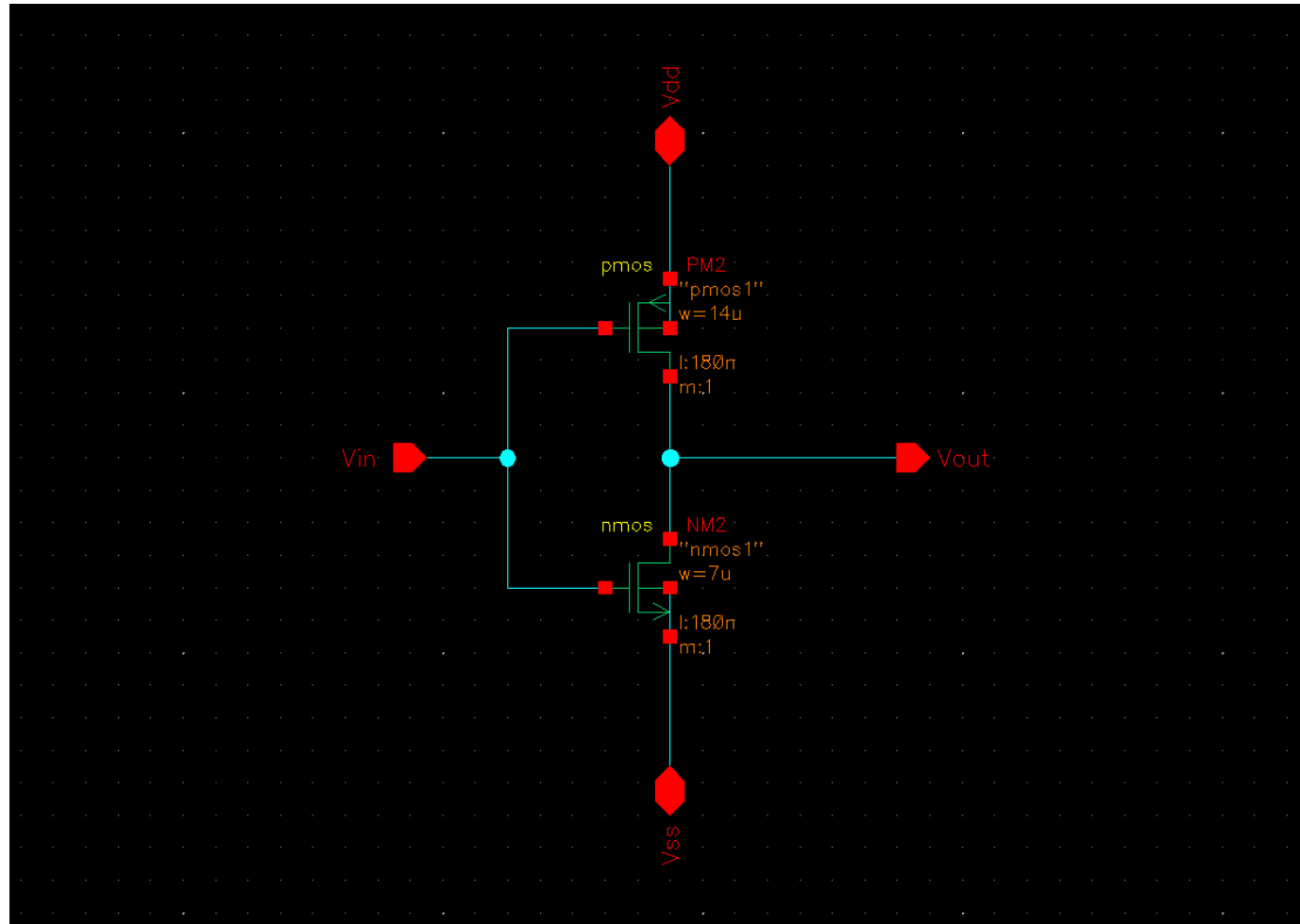


Fig-1 : Schematic of Inverter

A	Y
0	1
1	0

## Delay :

$$T_{on}=0.04ns$$

$$T_{off}=0.03ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$


$$T=0.03ns$$

## Transistors:

2 mosfets

# NAND:

$$Y=(A.B)'$$

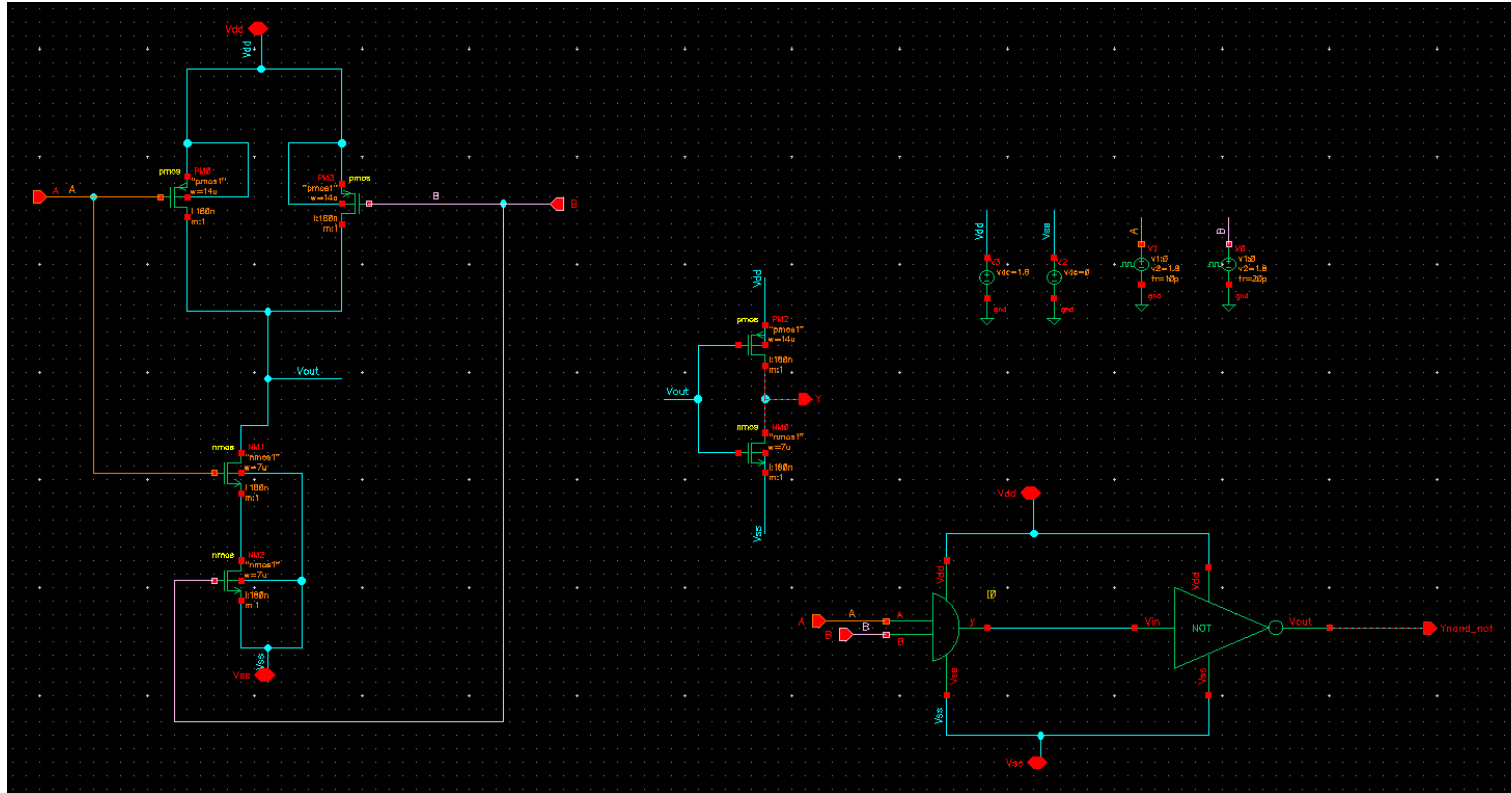

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

## Delay :

$$T_{on}=0.06ns$$

$$T_{off}=0.02ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.04ns$$

## Transistors:

4 mosfets

Fig-2 : Schematic of NAND

# AND:

$$Y=A.B$$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

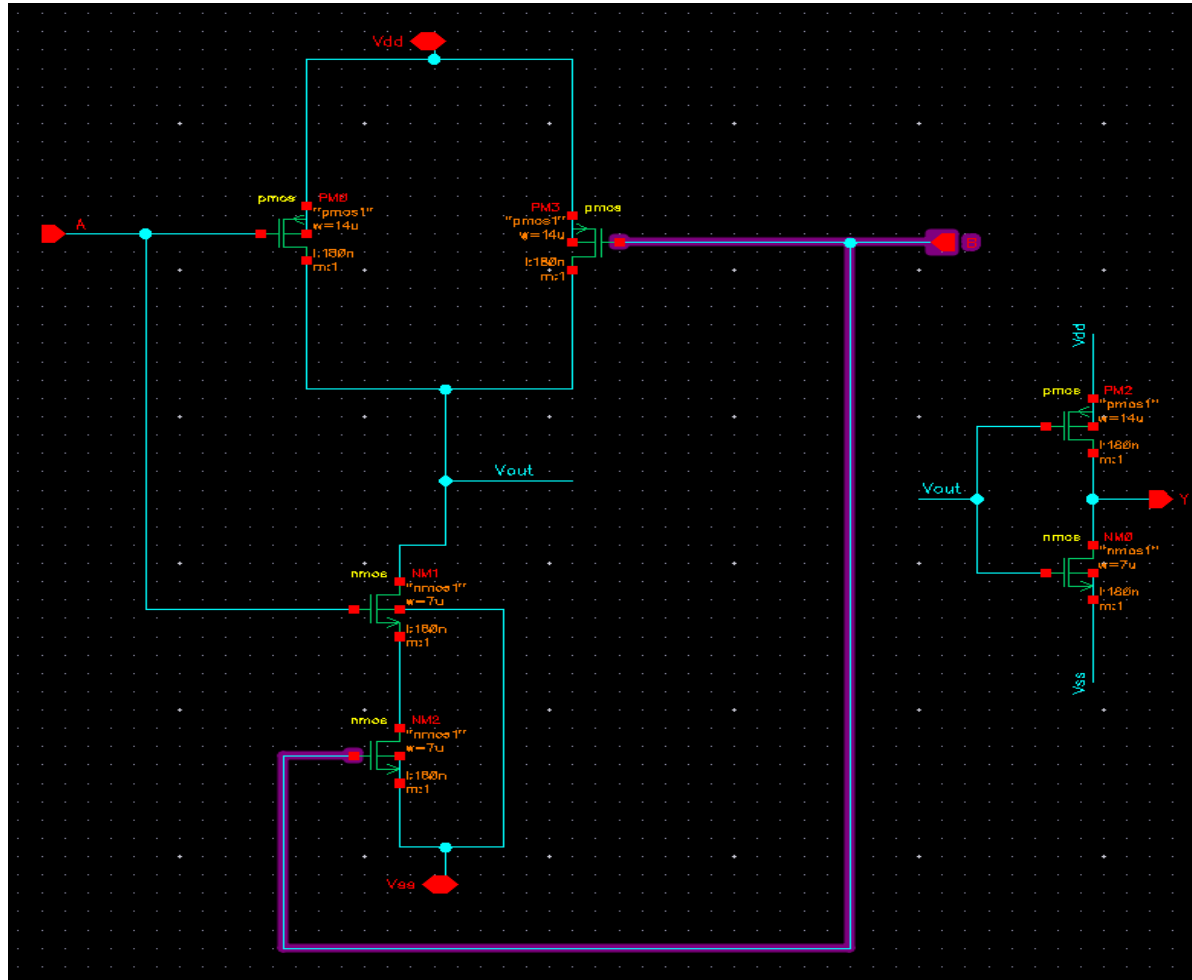


Fig-4 : Schematic of AND

**Delay :**

$$T_{on}=0.25ns$$

$$T_{off}=0.19ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.22ns$$

**Transistors:**

*6 mosfets*

# NOR:

$$Y=(A+B)'$$

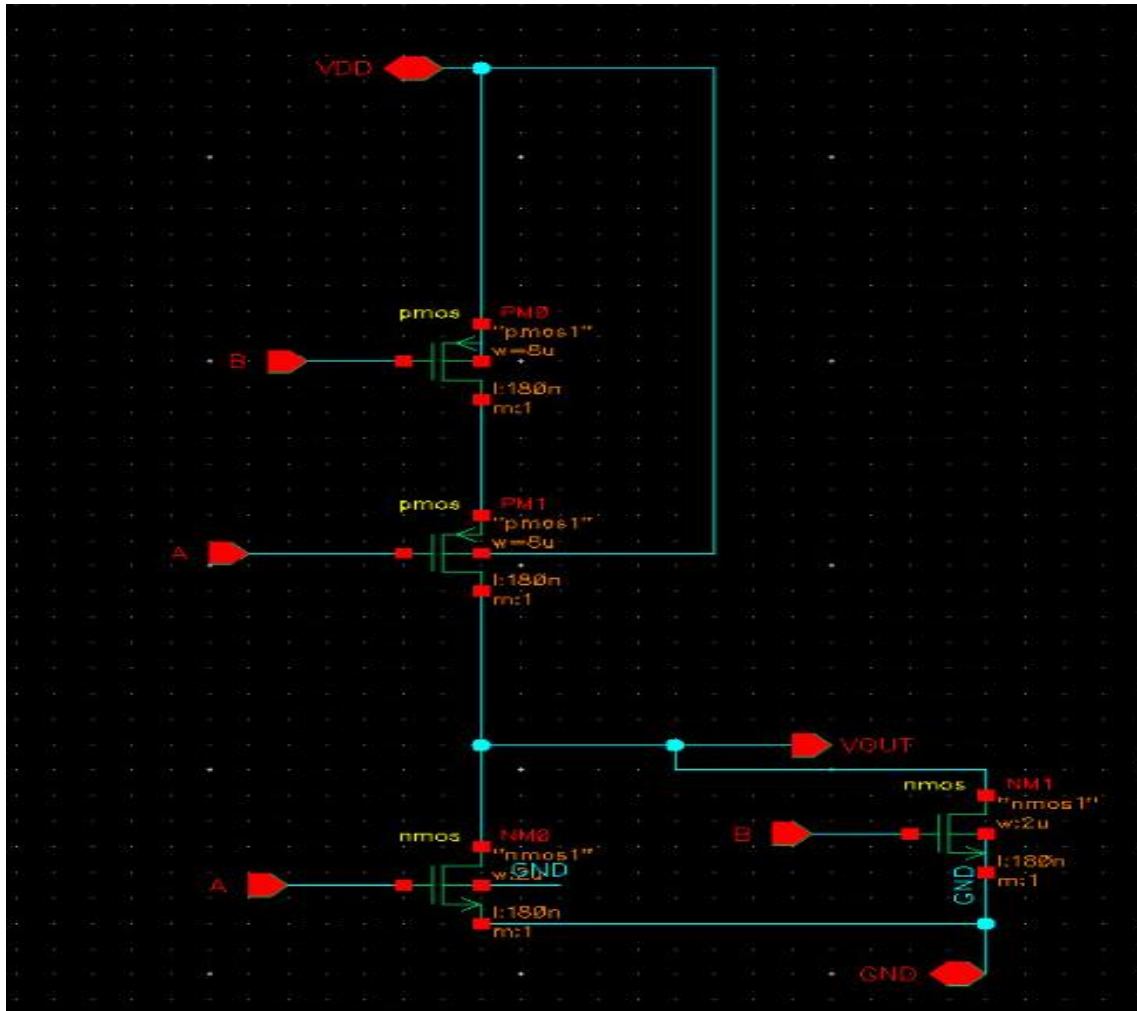


Fig-3 : Schematic of NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

## Delay :

$$T_{on}=0.060ns$$

$$T_{off}=0.067ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.0635ns$$

## Transistors:

4 mosfets



# OR:

$$Y=A+B$$

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

**Delay :**

$$T_{on}=0.3ns$$


$$T_{off}=0.25ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.27ns$$

**Transistors:**


*6 mosfets*

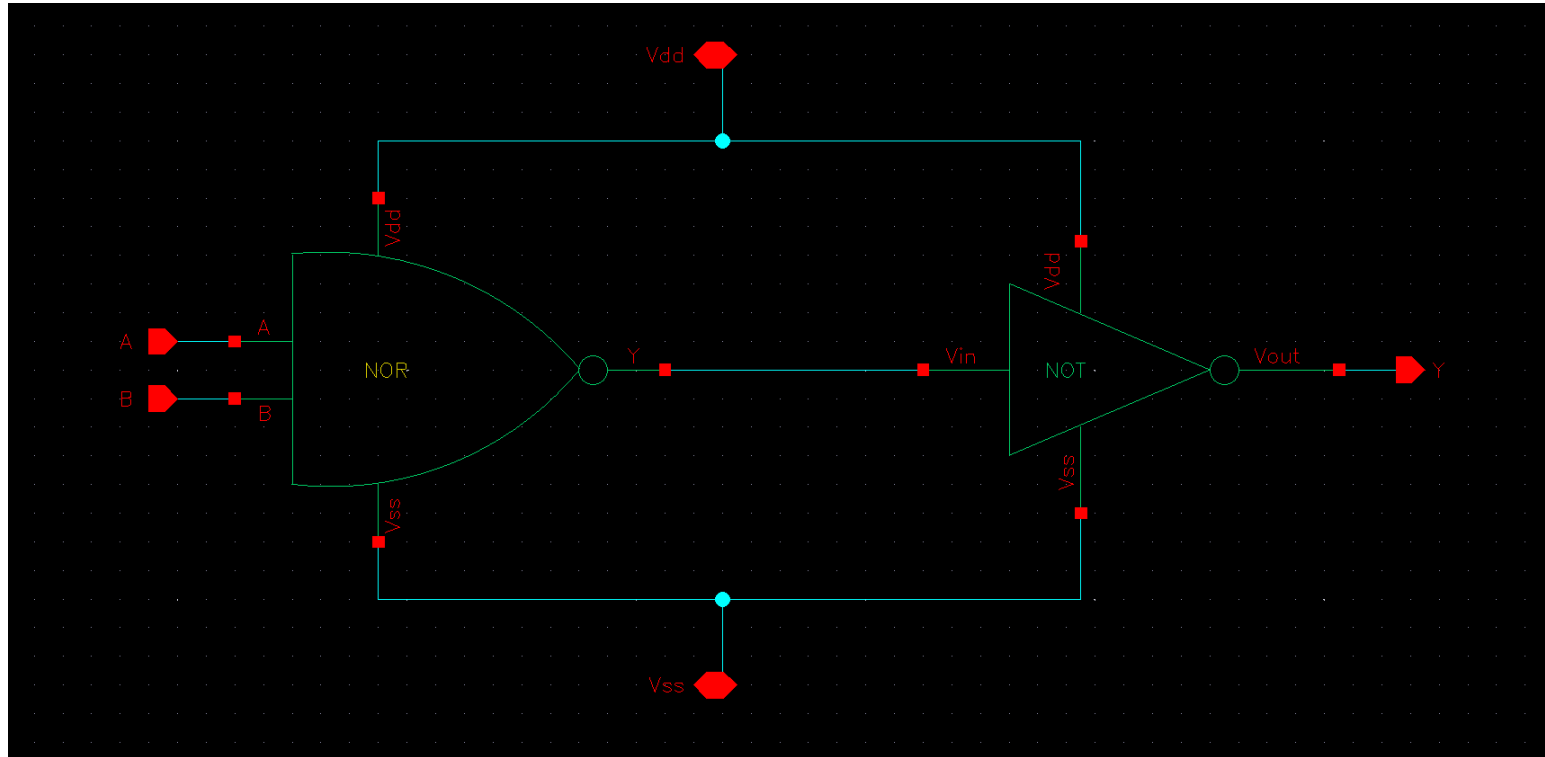

**Fig-5 : Schematic of OR**

# XOR:

$$Y=A'B + AB'$$

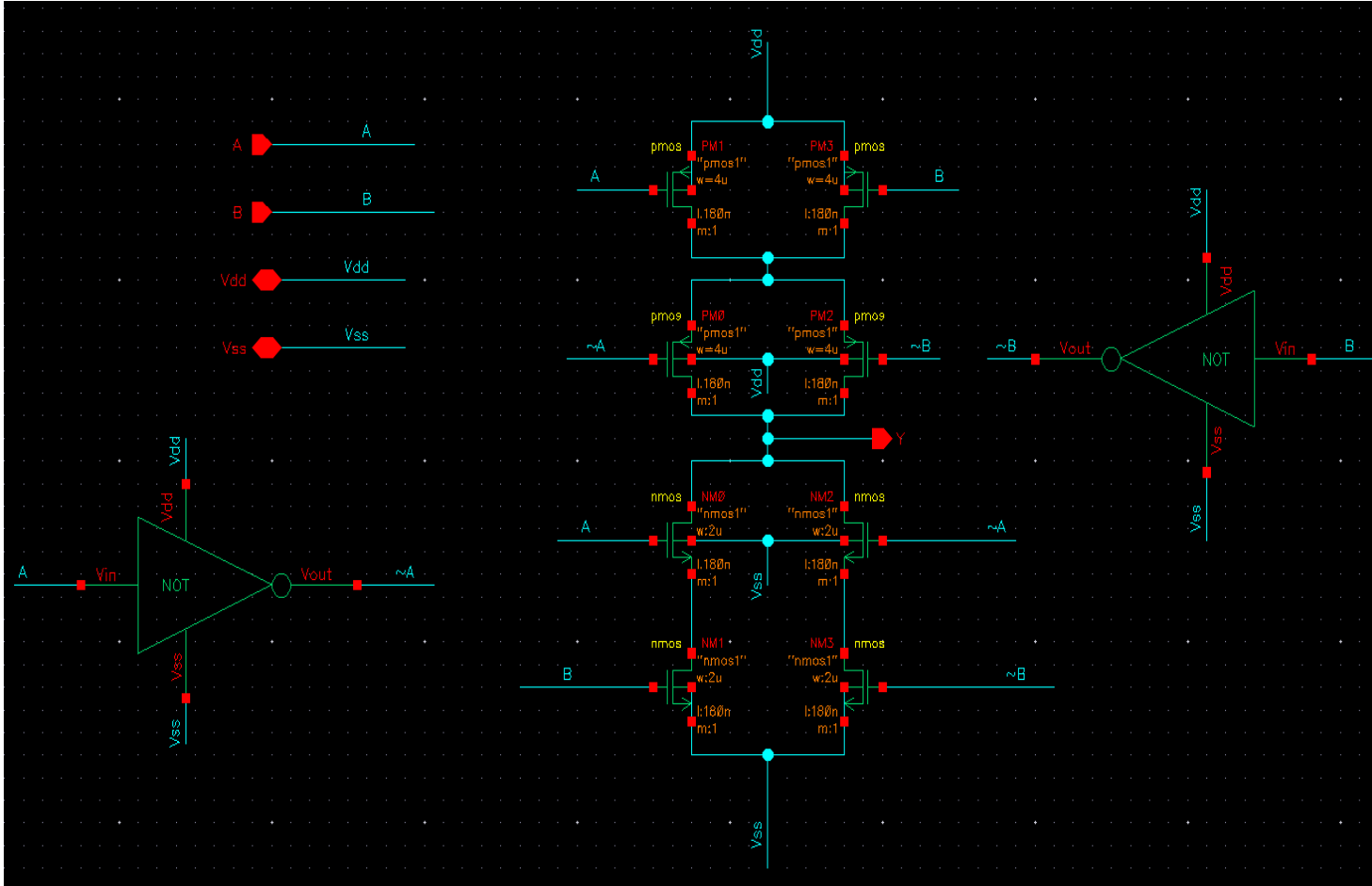

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

## Delay :

$$T_{on}=0.14ns$$

$$T_{off}=0.09ns$$

$$T = \frac{T_{on} + T_{off}}{2}$$

$$T=0.11ns$$

## Transistors:

*12 mosfets*

### Fig-6 : Schematic of XOR

# Half-Adder

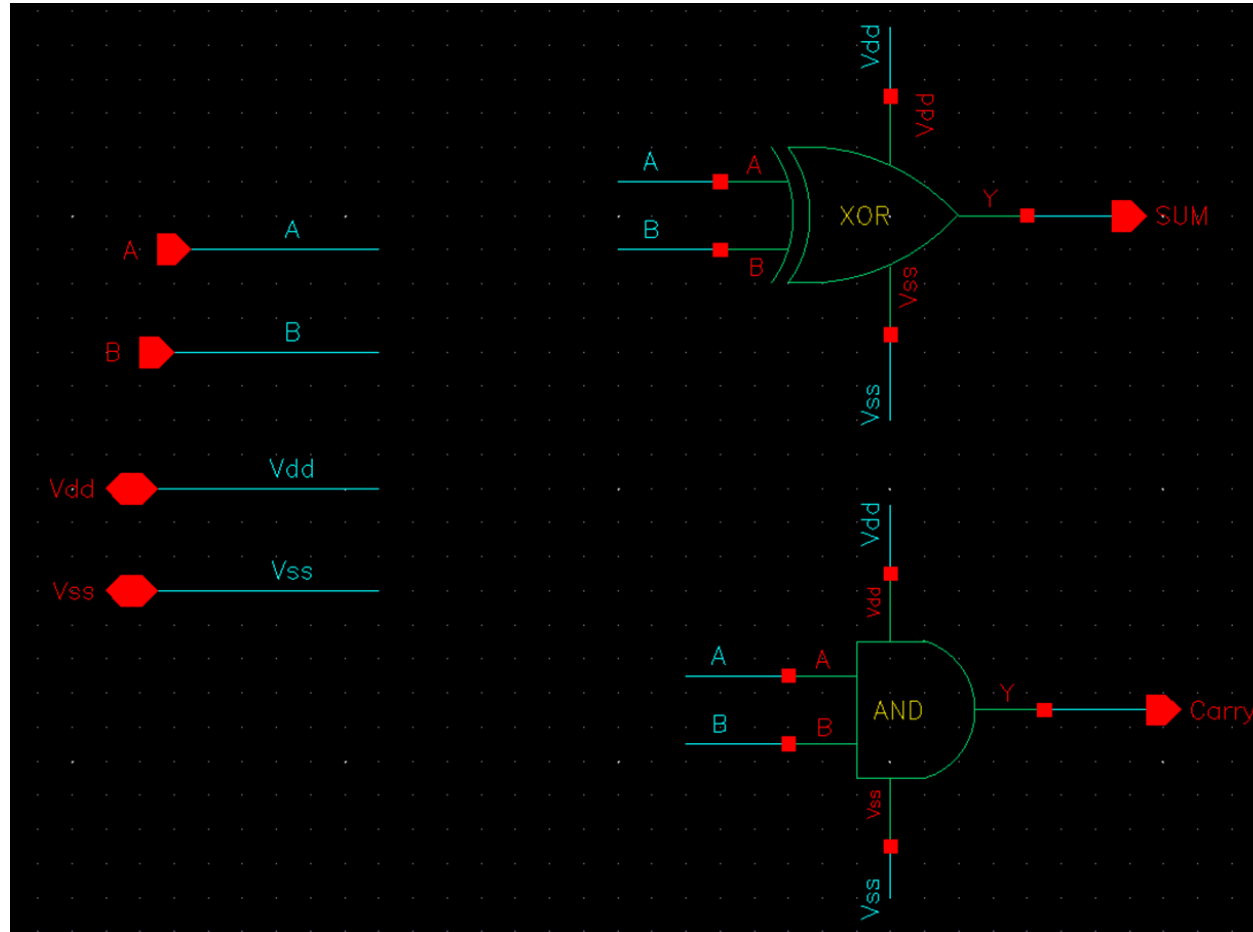


Fig-9 : Schematic of Half Adder

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A * B$$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

**Transistors:**

*20 mosfets*

# Output For Half- Adder:

 


Fig-10 : Output of Half-Adder

**Delay :**

**Sum:**

$$T_{on}=0.179ns$$

$$T_{off}=0.07ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.35ns$$

**Carry:**

$$T_{on}=0.07ns$$

$$T_{off}=0.06ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.065ns$$

# Full Adder

$$S = A \oplus B \oplus C_{in};$$
$$C_{out} = (A * B) + (C_{in} * (A \oplus B)).$$

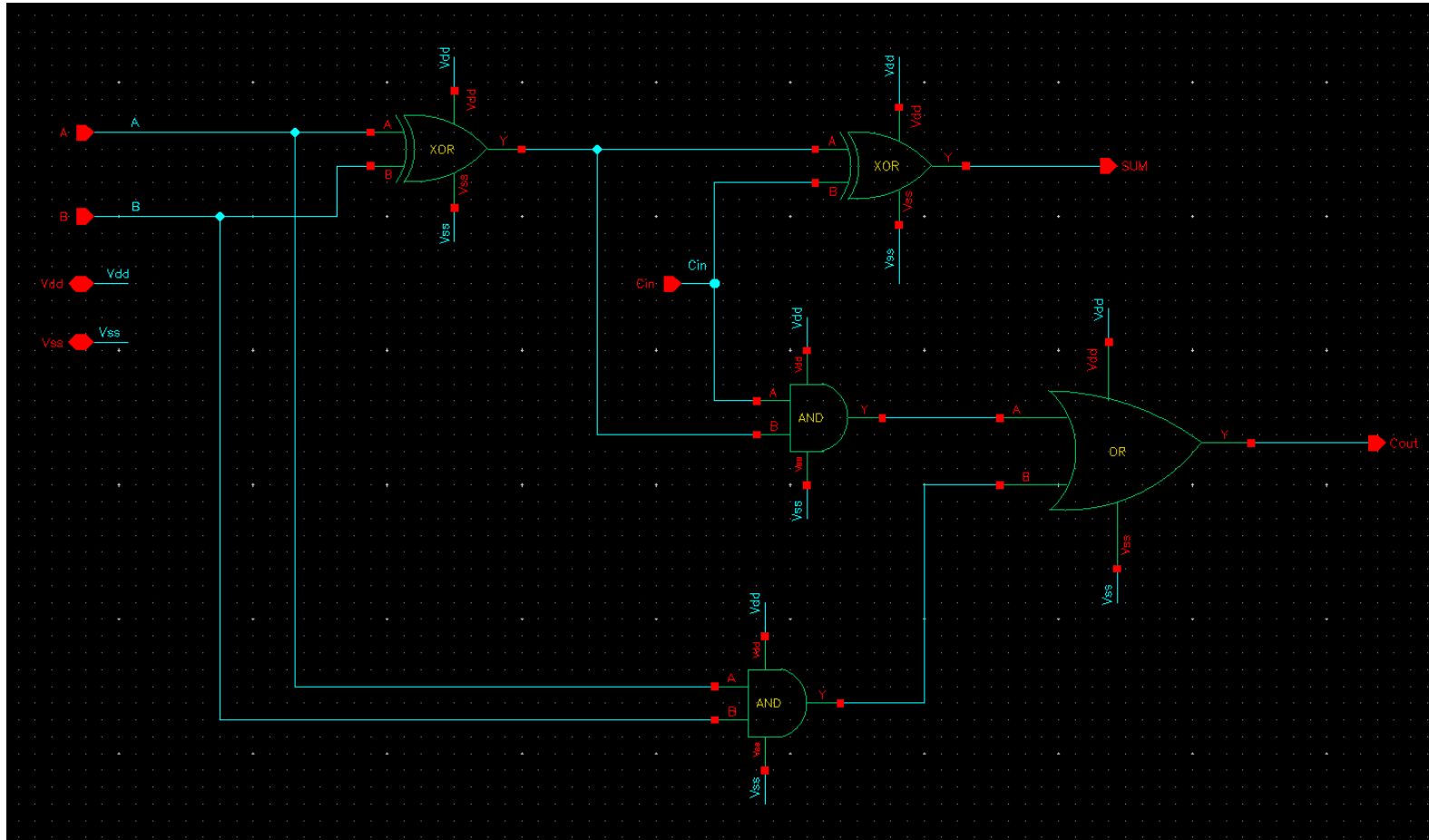


Fig-11 : Schematic of Full Adder

A	B	C	S	C <sub>O</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Transistors:**  
*48 mosfets*

# Output For Full Adder:

 


Fig-12 : Output of Full Adder

**Delay :**

**Sum:**

$$T_{on}=0.75ns$$

$$T_{off}=0.6ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.65ns$$

**Carry:**

$$T_{on}=0.15ns$$

$$T_{off}=0.2ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.17ns$$

# Full Adder Using Gates

$$S = A \oplus B \oplus C_{in};$$

$$C_{out} = (A * B) + (C_{in} * (A \oplus B)).$$

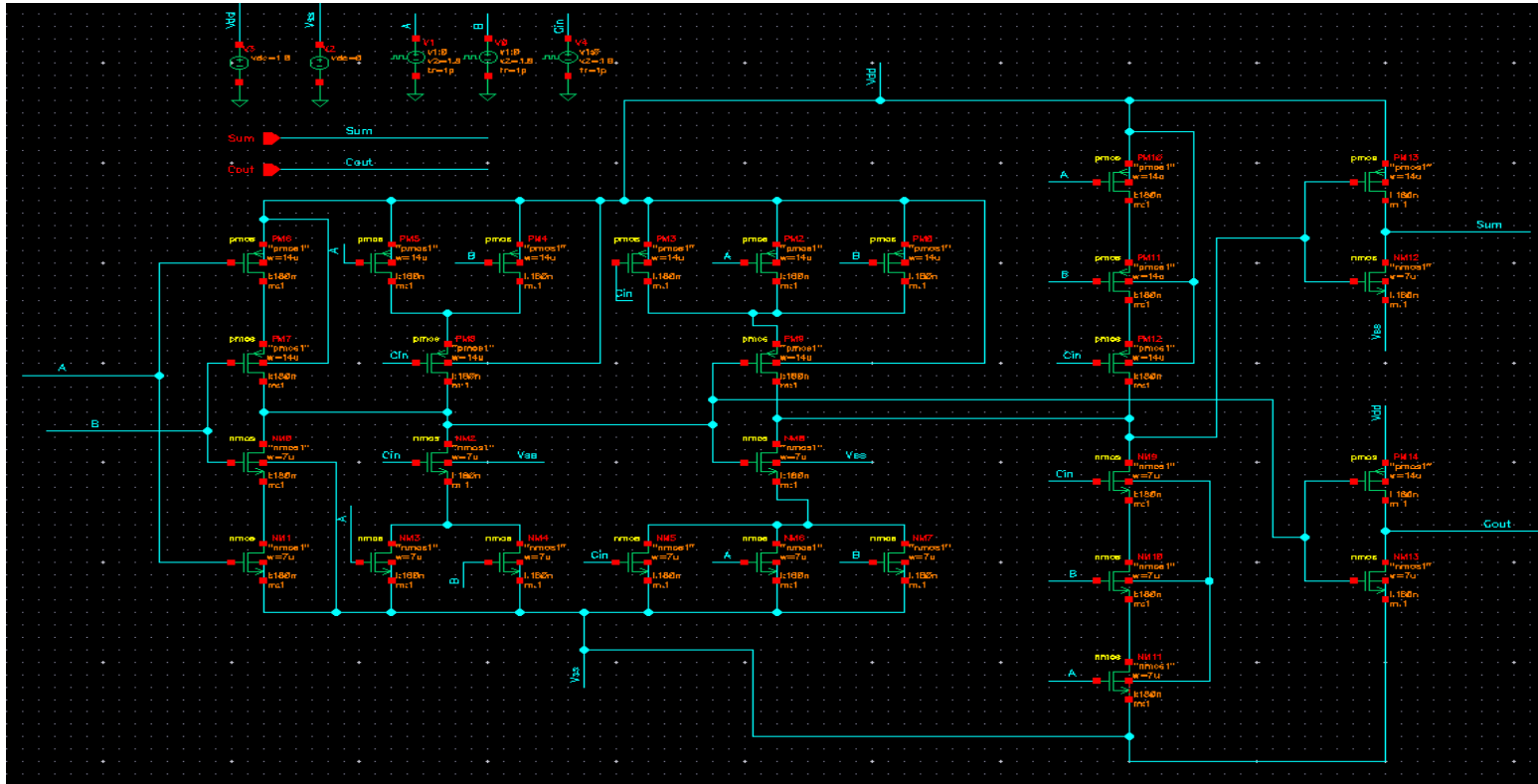


Fig-11 : Schematic of Full Adder

A	B	C	S	C0
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**Transistors:**  
*28 mosfets*

# Output For Full Adder Using Gates:

 


Fig-12 : Output of Full Adder

**Delay :**

**Sum:**

$$T_{on}=0.208ns$$

$$T_{off}=0.477ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.3425ns$$

**Carry:**

$$T_{on}=0.075ns$$

$$T_{off}=0.0069ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.072ns$$



# 4 Bit Multiplication Algorithm

b7 b6 b5 b4 b3 b2 b1 b0

a7 a6 a5 a4 a3 a2 a1 a0

a0b7 a0b6 a0b5 a0b4 a0b3 a0b2 a0b1 a0b0

a1b7 a1b6 a1b5 a1b4 a1b3 a1b2 a1b1 a1b0

a2b7 a2b6 a2b5 a2b4 a2b3 a2b2 a2b1 a2b0 c0

a3b7 a3b6 a3b5 a3b4 a3b3 a3b2 a3b1 a3b0 c1

a4b7 a4b6 a4b5 a4b4 a4b3 a4b2 a4b1 a4b0 c2

a5b7 a5b6 a5b5 a5b4 a5b3 a5b2 a5b1 a5b0 c3


a6b7 a6b6 a6b5 a6b4 a6b3 a6b2 a6b1 a6b0 c4

a7b7 a7b6 a7b5 a7b4 a7b3 a7b2 a7b1 a7b0 c5

c14 c13 c12 c11 c10 c9 c8 c7 c6

S15 S14 S13 S12 S11 S10 S9 S8 S7 S6 S5 S4 S3 S2 S1 S0

# 4 Bit Normal Multiplier:

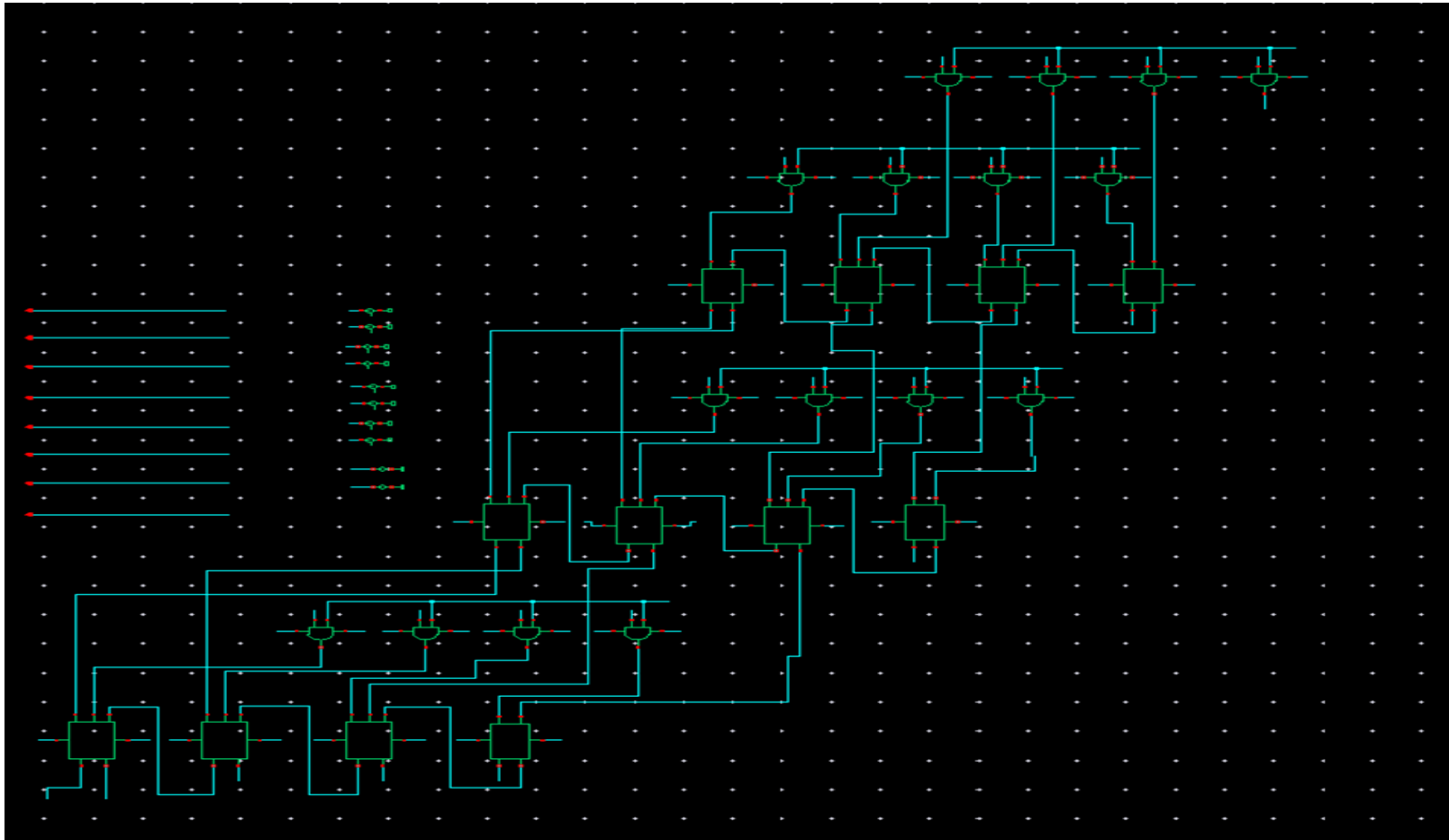

**Delay :**

$$T_{on}=0.14ns$$

$$T_{off}=0.09ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.11ns$$

**Transistors:**

*400 mosfets*

Fig-6 : 4 Bit Normal Multiplier

# Output For 4 Bit Multiplier :

 


Fig- 37: Output of 4 Bit Multiplier

# 4 Bit Vedic Multiplication Algorithm

 


Fig2: Algorithm of UT sutra

# 4 Bit Vedic Using Gates:

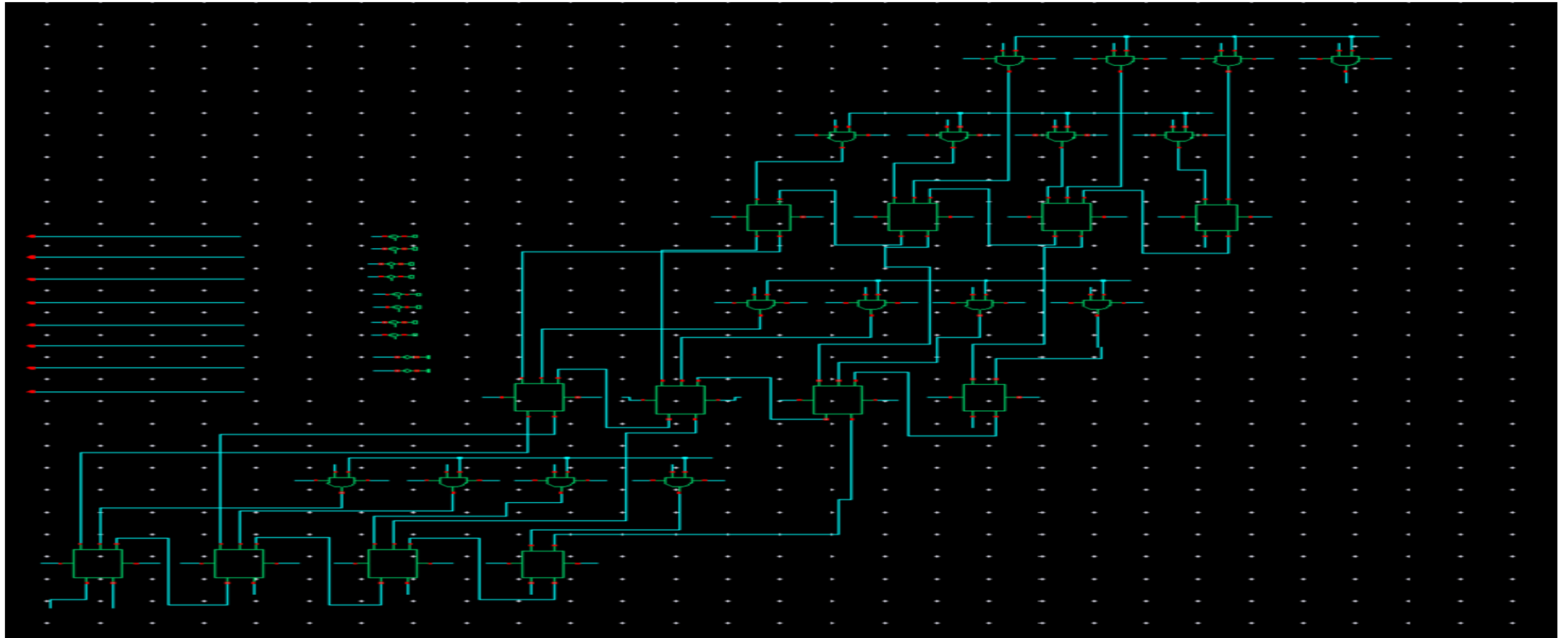


Fig-6 : 2 Bit Vedic Multiplier



# Output For 4 Bit Vedic Using Gates:

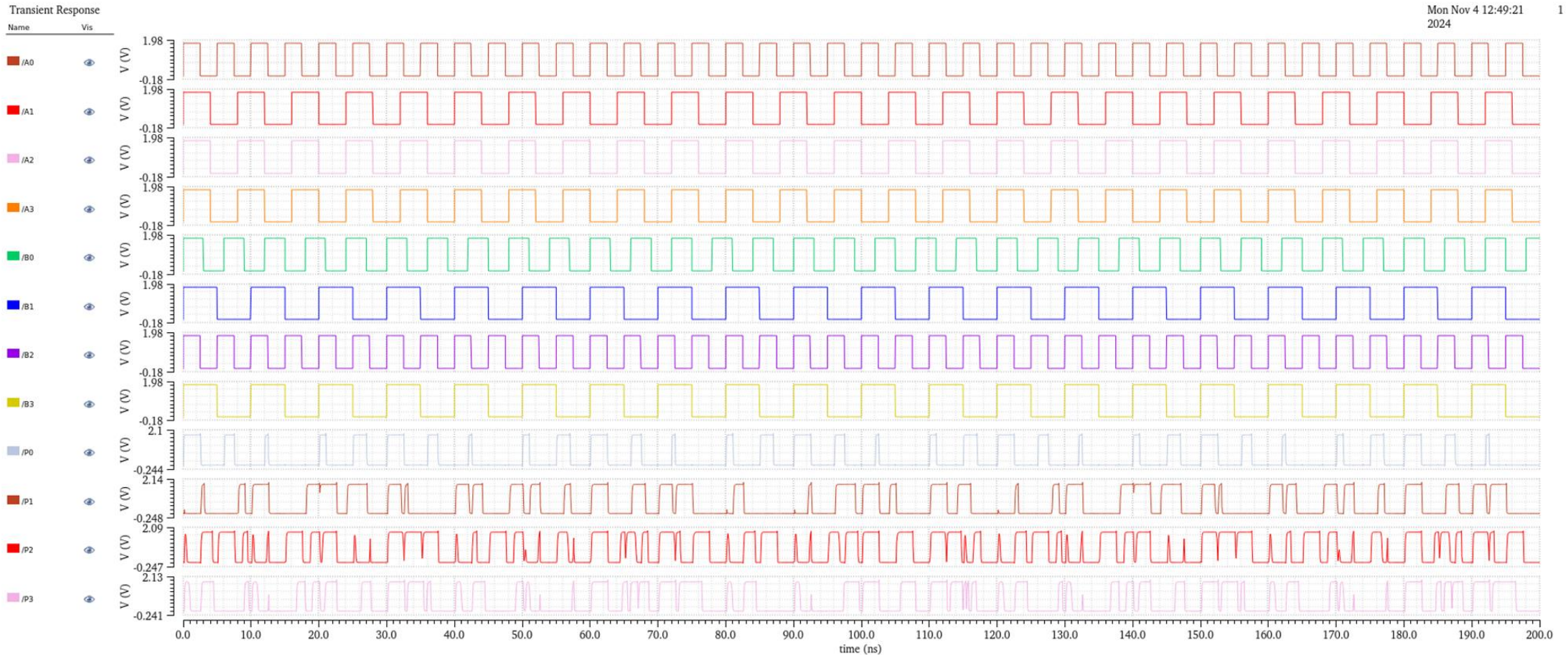


Fig- 37: Output of 8 Bit Multiplier

# 2 Bit Vedic Multiplier:

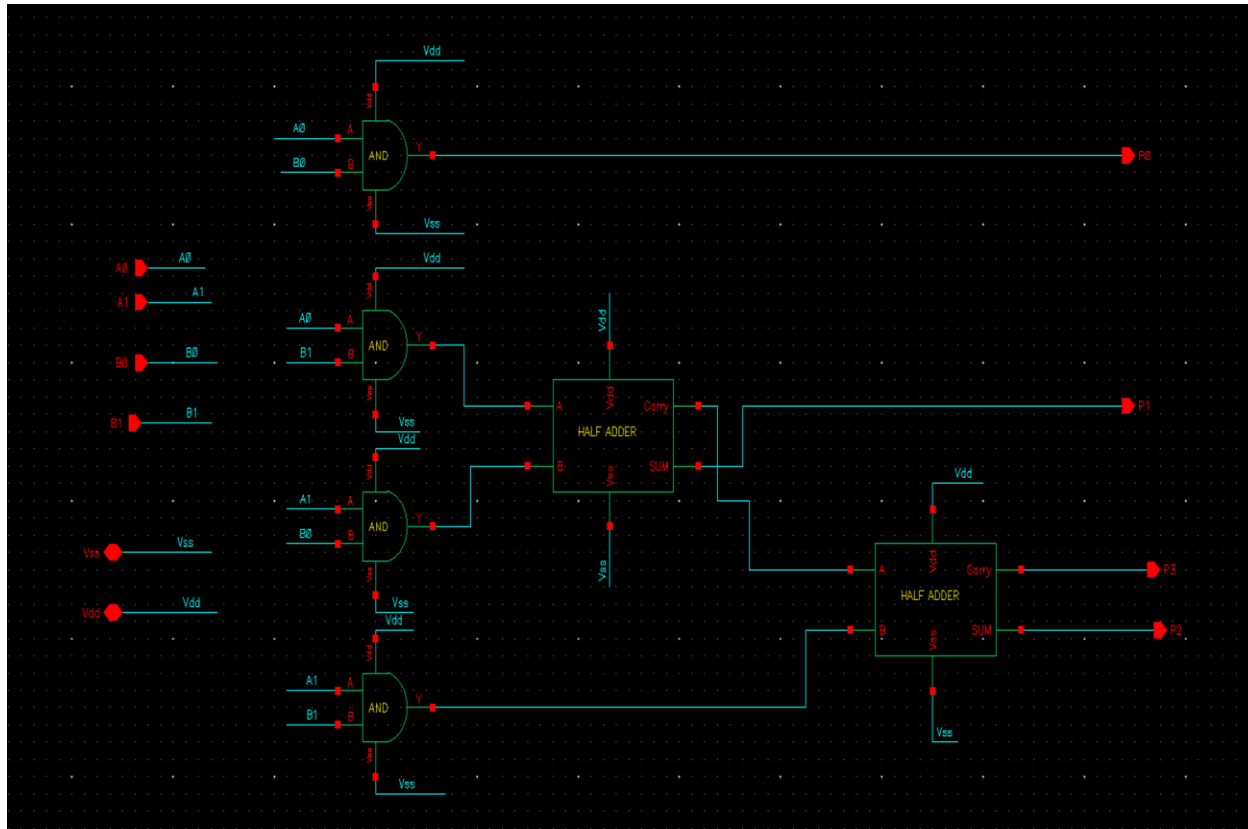


Fig-6 : 2 Bit Vedic Multiplier

**Delay :**

$$T_{on}=0.0344ns$$

$$T_{off}=0.107ns$$


$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.55ns$$

**Transistors:**

*64 mosfets*

## Output For 2 Bit Vedic Multiplier :

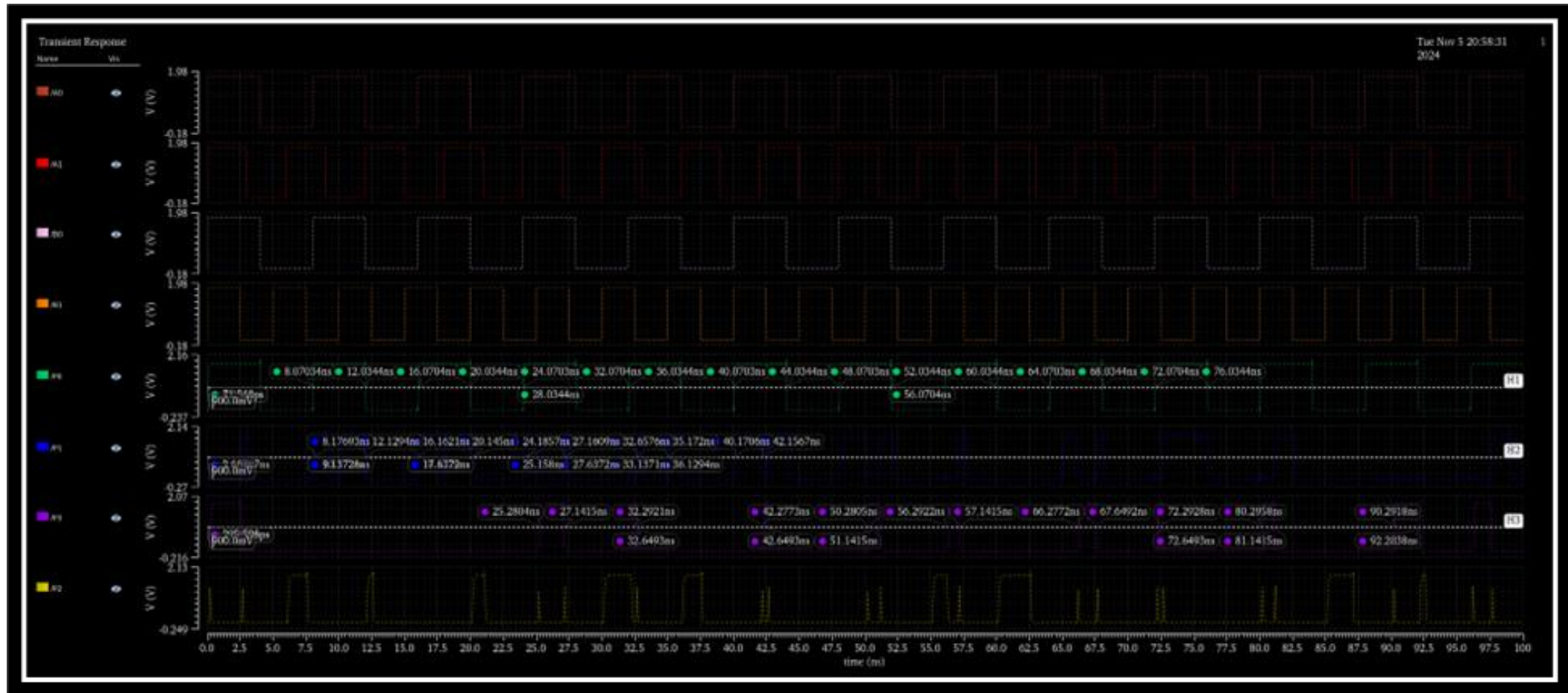

**Fig- 37: Output of 2 Bit Multiplier**



# 4 Bit RC Adder


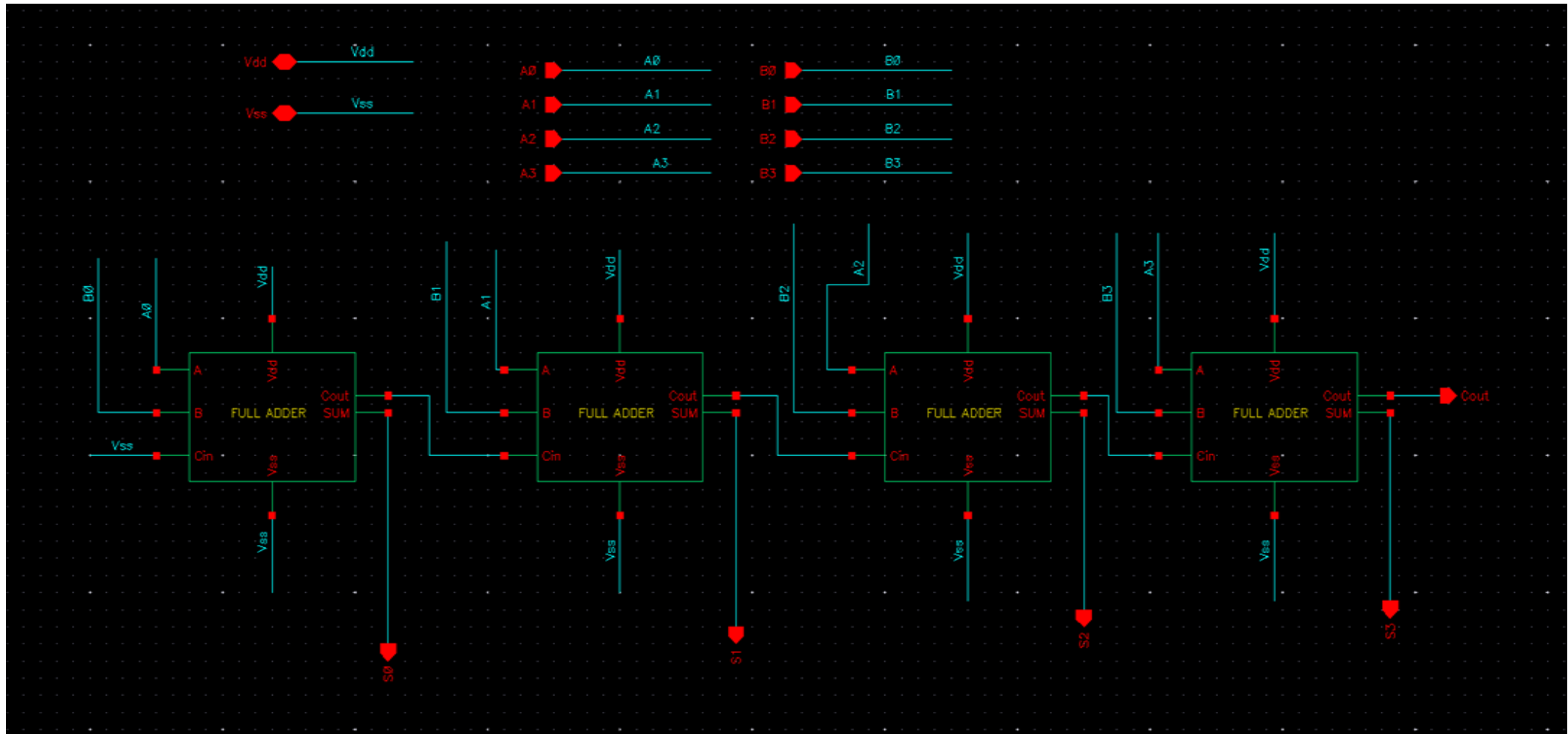


Fig-15 : Schematic of Adder

# Output For 4 Bit RC Adder :

 

**Delay :**

$$T_{on}=1.02ns$$

$$T_{off}=0.5ns$$

$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.75ns$$

**Transistors:**

*112 mosfets*

**Fig-16 : Output of 4 Bit Adder**

# 4 Bit Vedic Multiplier Using RCA

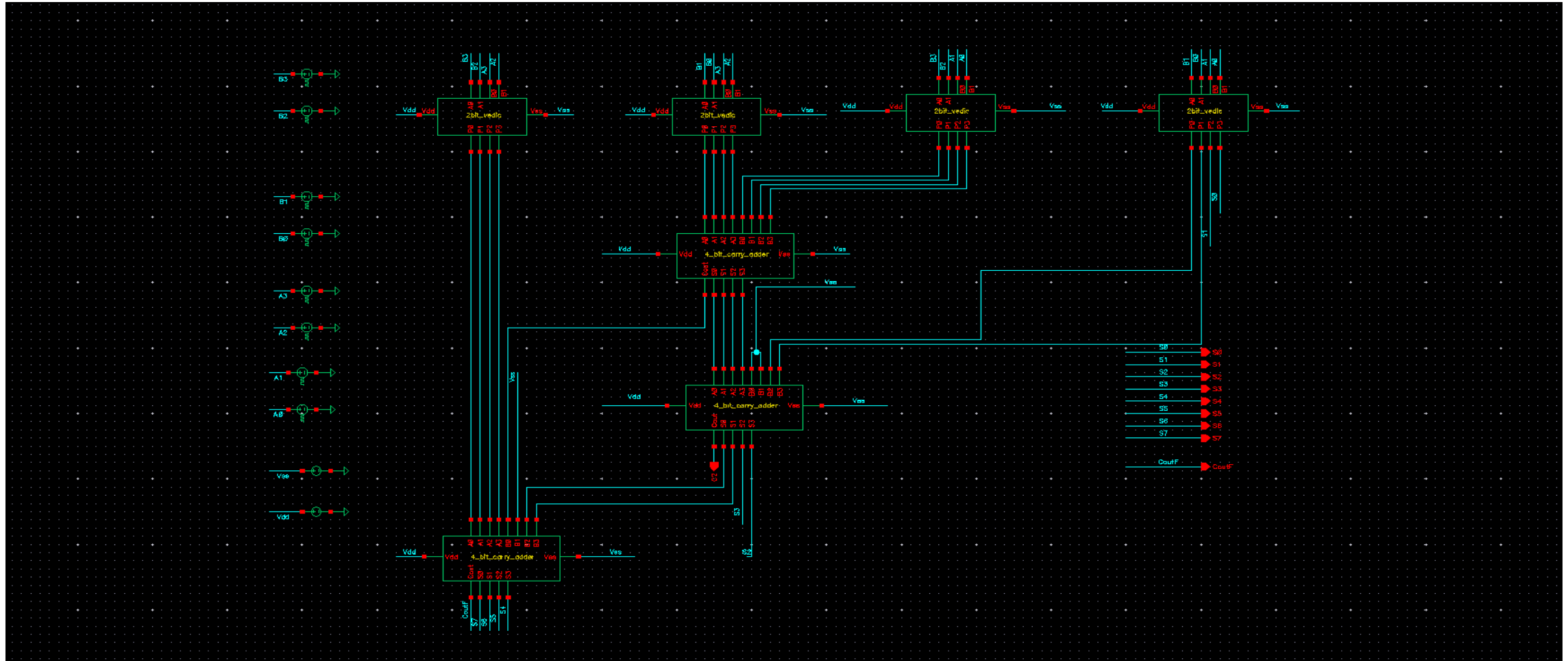


Fig-36 : Schematic of Multiplication

# 4 Bit Vedic Multiplier:

 


Fig-6 : Symbol of 4 Bit Vedic Multiplier

## Delay :

$$T_{on}=1.02ns$$

$$T_{off}=0.82ns$$


$$T=\frac{T_{on}+T_{off}}{2}$$

$$T=0.92ns$$

## Transistors:

*592 mosfets*

## Output For 4 Bit Vedic Using RCA Part1 :

 

**Fig- 37: Output of 8 Bit Multiplier**

# Output For 4 Bit Vedic Using RCA Part2 :


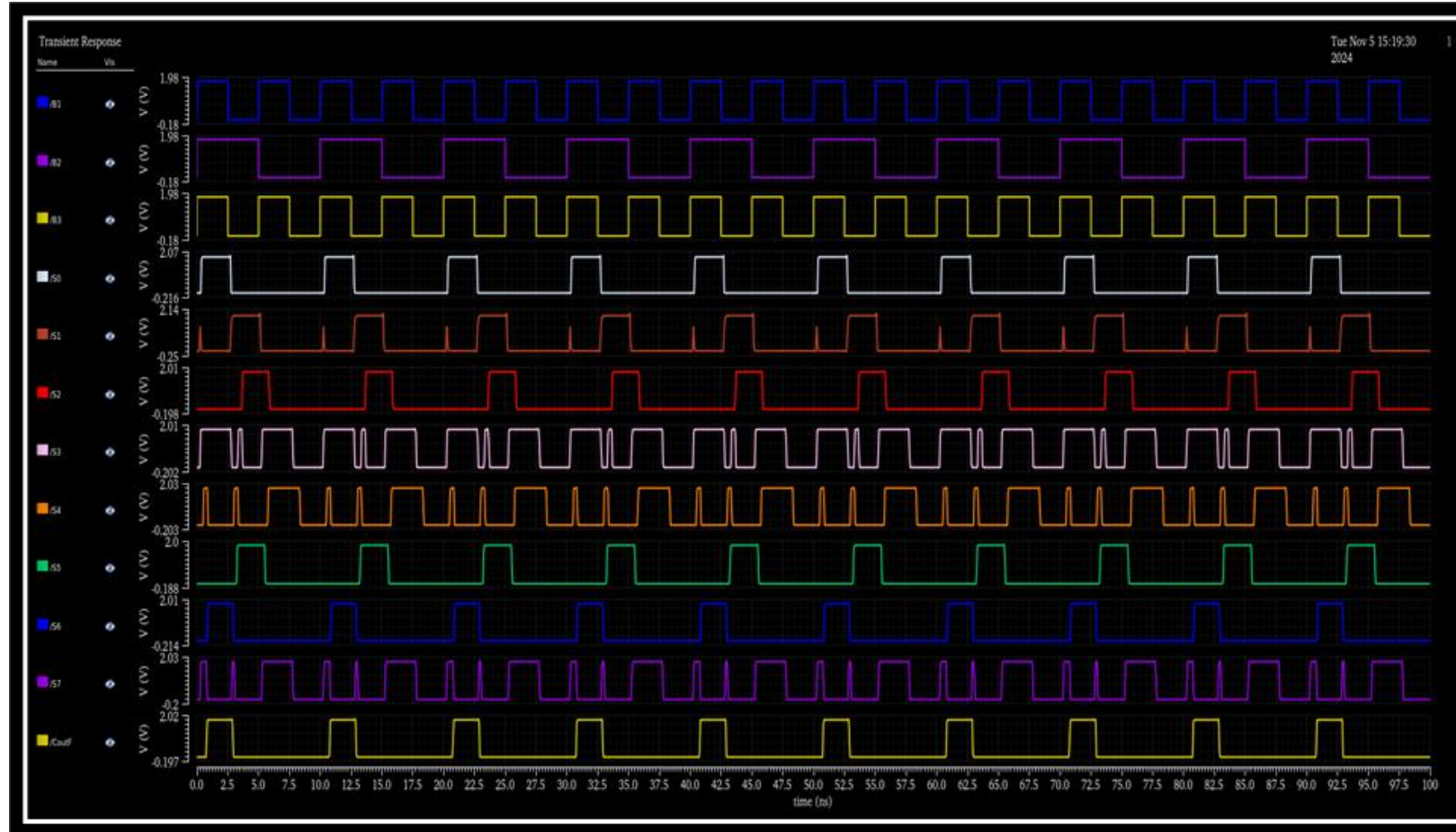


Fig- 37: Output of 8 Bit Multiplier

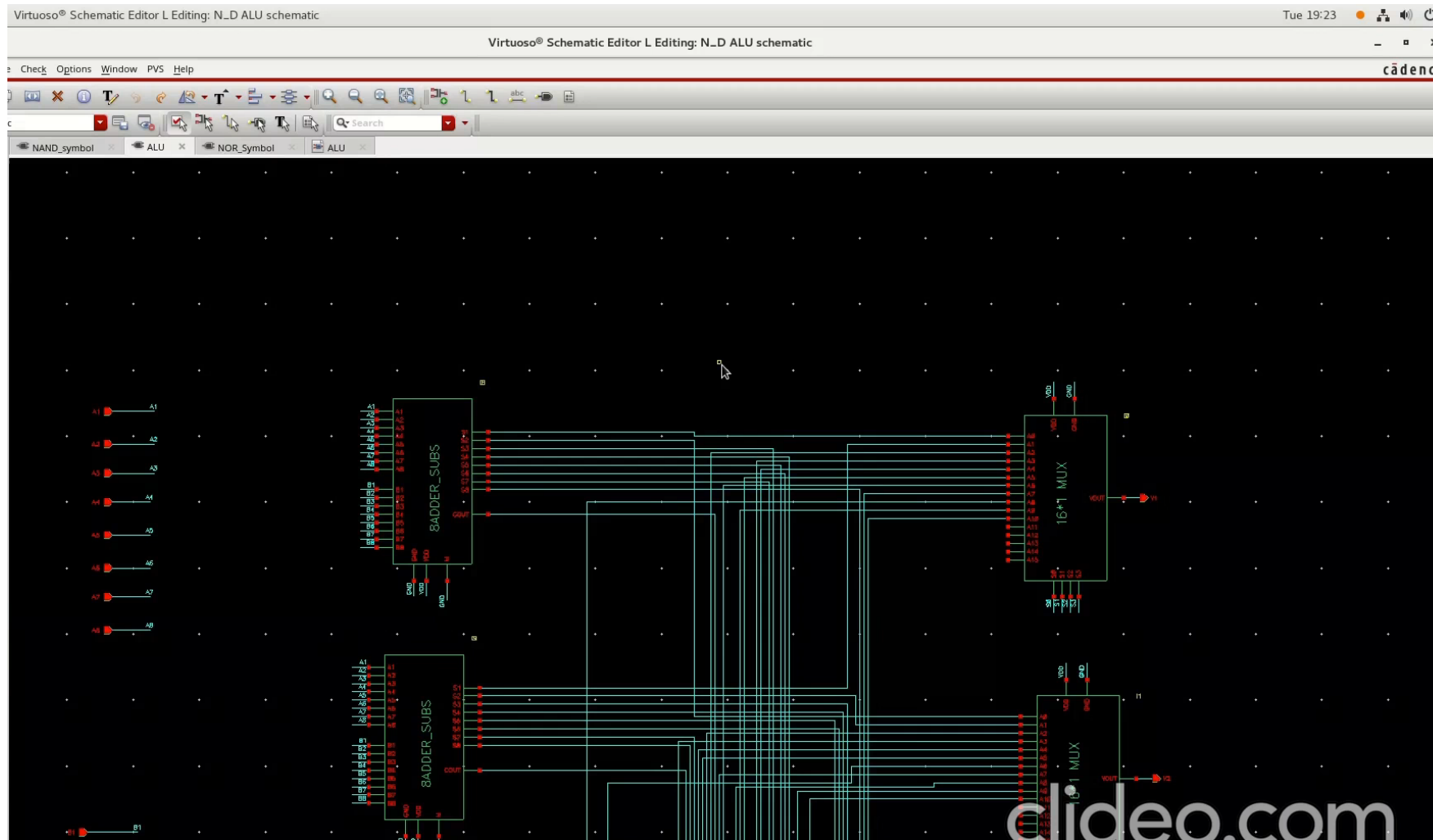

# 4 Bit Vedic Multiplier Demo Video :



# COMPARISON

Parameter	Delay (ns)	Power ( $\mu$ W)	PDP (pJ)
Inverter	0.03	13.3	0.399
NAND Gate	0.24	18.72	4.492
AND Gate	0.22	28.32	6.23
OR Gate	0.27	32.18	8.688
XOR Gate	0.11	42.53	4.67
Half Adder	0.35	84.82	29.6
Full Adder	0.65	220.41	143.19
2-bit vedic Multiplier	0.5	140.58	70.25
4 -bit VedicType 1	1.43	1429	2043.47
4 -bit Vedic Type 2	0.92	1138	1046.96



# APPLICATIONS

- It is used in DSP applications
- It is used for filters and Fourier Transform
- It is also used in ALU
- Embedded Systems
- Communications system in QAM , OFDM
- Machine Learning Matrix Multiplication
- Control System Controller design

**Thank You....!**